 


W6/7B: DE [Brainstorm] 2.4.1 Date of Birth Combinational Logic Circuit Design

Equipment

Calculator (preferably one with a number base conversion feature)
Computer with Circuit Design Software (CDS)
Breadboarding Hardware or Digital MiniSystem

- Integrated Circuits:
 - 74LS04 (Hex Inverter gates)
 - 74LS08 (Quad AND gates)
 - 74LS32 (Quad OR gates)
 - 74LS00 (Quad NAND gates)
 - 74LS02 (Quad NOR gates)
- 22-gauge solid wire
- Multipurpose Wire Stripper



Procedure

- Design a combinational logic circuit that has three inputs and seven outputs. When the inputs (X, Y, and Z) create a count from 000 to 111, the seven outputs (a through g) generate the logic required to display your date of birth on a seven-segment display (SSD).

Aeries Screenshot

Last Name	First Name	Middle Name	Suffix	Grd	Age	Birthdate
Jeide	Matthew	Alexander	Jr	11	17	12/12/2007

- The date of birth will be displayed in the **MM-DD-YY** format. For example, if you were born on May 12, 2001, your design will display **05-12-01**.

x	y	z	Display	a	b	c	d	e	f	g
0	0	0	1	0	1	1	0	0	0	0
0	0	1	2	1	1	0	1	1	0	1
0	1	0	—	0	0	0	0	0	0	1
0	1	1	1	0	1	1	0	0	0	0
1	0	0	2	1	1	0	1	1	0	1
1	0	1	—	0	0	0	0	0	0	1
1	1	0	0	1	1	1	1	1	1	0
1	1	1	7	1	1	1	0	0	0	0

Jeide, Matthew

Date 2/7/2025

Period 2


<table><tr><th>a</th><th>\bar{z}</th><th>z</th></tr><tr><td>$\bar{x}\bar{y}$</td><td>0</td><td>1</td></tr><tr><td>$\bar{x}y$</td><td>0</td><td>0</td></tr><tr><td>xy</td><td>1</td><td>1</td></tr><tr><td>$x\bar{y}$</td><td>1</td><td>0</td></tr></table>	a	\bar{z}	z	$\bar{x}\bar{y}$	0	1	$\bar{x}y$	0	0	xy	1	1	$x\bar{y}$	1	0	<table><tr><th>b</th><th>\bar{z}</th><th>z</th></tr><tr><td>$\bar{x}\bar{y}$</td><td>1</td><td>1</td></tr><tr><td>$\bar{x}y$</td><td>0</td><td>1</td></tr><tr><td>xy</td><td>1</td><td>1</td></tr><tr><td>$x\bar{y}$</td><td>1</td><td>0</td></tr></table>	b	\bar{z}	z	$\bar{x}\bar{y}$	1	1	$\bar{x}y$	0	1	xy	1	1	$x\bar{y}$	1	0	<table><tr><th>c</th><th>\bar{z}</th><th>z</th></tr><tr><td>$\bar{x}\bar{y}$</td><td>1</td><td>0</td></tr><tr><td>$\bar{x}y$</td><td>0</td><td>1</td></tr><tr><td>xy</td><td>1</td><td>1</td></tr><tr><td>$x\bar{y}$</td><td>0</td><td>0</td></tr></table>	c	\bar{z}	z	$\bar{x}\bar{y}$	1	0	$\bar{x}y$	0	1	xy	1	1	$x\bar{y}$	0	0	<table><tr><th>d</th><th>\bar{z}</th><th>z</th></tr><tr><td>$\bar{x}\bar{y}$</td><td>0</td><td>1</td></tr><tr><td>$\bar{x}y$</td><td>0</td><td>0</td></tr><tr><td>xy</td><td>1</td><td>0</td></tr><tr><td>$x\bar{y}$</td><td>1</td><td>0</td></tr></table>	d	\bar{z}	z	$\bar{x}\bar{y}$	0	1	$\bar{x}y$	0	0	xy	1	0	$x\bar{y}$	1	0
a	\bar{z}	z																																																													
$\bar{x}\bar{y}$	0	1																																																													
$\bar{x}y$	0	0																																																													
xy	1	1																																																													
$x\bar{y}$	1	0																																																													
b	\bar{z}	z																																																													
$\bar{x}\bar{y}$	1	1																																																													
$\bar{x}y$	0	1																																																													
xy	1	1																																																													
$x\bar{y}$	1	0																																																													
c	\bar{z}	z																																																													
$\bar{x}\bar{y}$	1	0																																																													
$\bar{x}y$	0	1																																																													
xy	1	1																																																													
$x\bar{y}$	0	0																																																													
d	\bar{z}	z																																																													
$\bar{x}\bar{y}$	0	1																																																													
$\bar{x}y$	0	0																																																													
xy	1	0																																																													
$x\bar{y}$	1	0																																																													
<table><tr><th>e</th><th>\bar{z}</th><th>z</th></tr><tr><td>$\bar{x}\bar{y}$</td><td>0</td><td>1</td></tr><tr><td>$\bar{x}y$</td><td>0</td><td>0</td></tr><tr><td>xy</td><td>1</td><td>0</td></tr><tr><td>$x\bar{y}$</td><td>1</td><td>0</td></tr></table>	e	\bar{z}	z	$\bar{x}\bar{y}$	0	1	$\bar{x}y$	0	0	xy	1	0	$x\bar{y}$	1	0	<table><tr><th>f</th><th>\bar{z}</th><th>z</th></tr><tr><td>$\bar{x}\bar{y}$</td><td>0</td><td>0</td></tr><tr><td>$\bar{x}y$</td><td>0</td><td>0</td></tr><tr><td>xy</td><td>1</td><td>0</td></tr><tr><td>$x\bar{y}$</td><td>0</td><td>0</td></tr></table>	f	\bar{z}	z	$\bar{x}\bar{y}$	0	0	$\bar{x}y$	0	0	xy	1	0	$x\bar{y}$	0	0	<table><tr><th>g</th><th>\bar{z}</th><th>z</th></tr><tr><td>$\bar{x}\bar{y}$</td><td>0</td><td>1</td></tr><tr><td>$\bar{x}y$</td><td>1</td><td>0</td></tr><tr><td>xy</td><td>0</td><td>0</td></tr><tr><td>$x\bar{y}$</td><td>1</td><td>1</td></tr></table>	g	\bar{z}	z	$\bar{x}\bar{y}$	0	1	$\bar{x}y$	1	0	xy	0	0	$x\bar{y}$	1	1	<p>Equations</p> <p>a. $X\bar{Z} + XY + \bar{X}\bar{Y}Z$</p> <p>b. $\bar{X}\bar{Y} + \bar{X}Z + XY$</p> <p>c. $XY + \bar{Z}\bar{Y}\bar{X} + Z\bar{X}Y$</p> <p>d. $X\bar{Z} + \bar{X}\bar{Y}Z$</p> <p>e. $X\bar{Z} + \bar{X}\bar{Y}Z$</p> <p>f. $XY\bar{Z}$</p> <p>g. $X\bar{Y} + \bar{X}Y\bar{Z} + \bar{X}\bar{Y}Z$</p>															
e	\bar{z}	z																																																													
$\bar{x}\bar{y}$	0	1																																																													
$\bar{x}y$	0	0																																																													
xy	1	0																																																													
$x\bar{y}$	1	0																																																													
f	\bar{z}	z																																																													
$\bar{x}\bar{y}$	0	0																																																													
$\bar{x}y$	0	0																																																													
xy	1	0																																																													
$x\bar{y}$	0	0																																																													
g	\bar{z}	z																																																													
$\bar{x}\bar{y}$	0	1																																																													
$\bar{x}y$	1	0																																																													
xy	0	0																																																													
$x\bar{y}$	1	1																																																													

Insert a screenshot of your Brainstorm Design a-g.

Jeide, Matthew

Date 2/7/2025

Period 2

 

3. Detailed Design Specifications:

- The SSD must be a common cathode.
- Current limiting resistors ($150\ \Omega$ — $270\ \Omega$) must be used.
- The Karnaugh mapping technique must be used to obtain the simplified logic expression for each of the seven segments.

Insert your Karnaugh mapping technique and a logical expression for each of the seven segments. Make sure to include all truth tables and logic expressions.

DOB Truth Table

X	Y	Z	D
0	0	0	1
0	0	1	2
0	1	0	-
0	1	1	1
1	0	0	2
1	0	1	-
1	1	0	0
1	1	1	7

A	B	C	D	E	F	G
0	1	1	0	0	0	0
1	1	0	1	1	0	1
0	0	0	0	0	0	1
0	1	1	0	0	0	0
1	1	0	1	1	0	1
0	0	0	0	0	0	1
1	1	1	1	1	1	0
1	1	1	0	0	0	0

RECEIVED
FEB 11 2025

Segment A

$\bar{X}\bar{Y}$	$\bar{X}Y$	$X\bar{Y}$	XY
0	0	1	1
0	0	0	0
1	1	1	1
1	1	1	0

$$X\bar{Z} + XY + X\bar{Y}Z$$

Segment B

$\bar{X}\bar{Y}$	$\bar{X}Y$	$X\bar{Y}$	XY
1	1	0	1
0	0	1	1
1	1	1	1
1	1	0	0

$$\bar{X}\bar{Y} + \bar{X}Z + X\bar{Z} + XY$$

Segment C

$\bar{X}\bar{Y}$	$\bar{X}Y$	$X\bar{Y}$	XY
1	1	0	1
0	0	1	1
1	1	1	1
0	0	0	0

$$XY + \bar{Z}\bar{X}\bar{Y} + Z\bar{X}Y$$

Segment D & E

$\bar{X}\bar{Y}$	$\bar{X}Y$	$X\bar{Y}$	XY
0	1	0	1
0	0	1	0
1	1	1	0
1	1	0	0

$$XZ + \bar{X}\bar{Y}Z$$

Segment F

$$XY\bar{Z}$$

Segment G

$\bar{X}\bar{Y}$	$\bar{X}Y$	$X\bar{Y}$	XY
0	1	1	0
0	0	1	0
1	1	1	1
1	1	1	1

$$X\bar{Y} + \bar{X}Y\bar{Z} + X\bar{Y}Z$$

d. At least one segment must be implemented with NAND only logic.

e. At least one segment must be implemented with NOR only logic.

f. The implementation of the remaining segments is your choice.

Simulation

Using the Circuit Design Software (CDS), enter and test your Date of Birth design.

Jeide, Matthew


Date 2/7/2025

Period 2

- g. Use switches for the inputs X, Y, and Z.
- h. If two SSD pins share the same input, you may need to reduce the resistance to get the segment to display.
- i. Verify that the circuit is working as designed.
- j. If the circuit is not working properly, review your design work and circuit implementation to identify your mistake. Make any necessary corrections and retest.
- k. Be sure to document all changes in your engineering notebook.

Insert a screenshot and video of the Multisim design [EX: MM-DD-YY format]

https://youtu.be/_6YM0bM2M5s

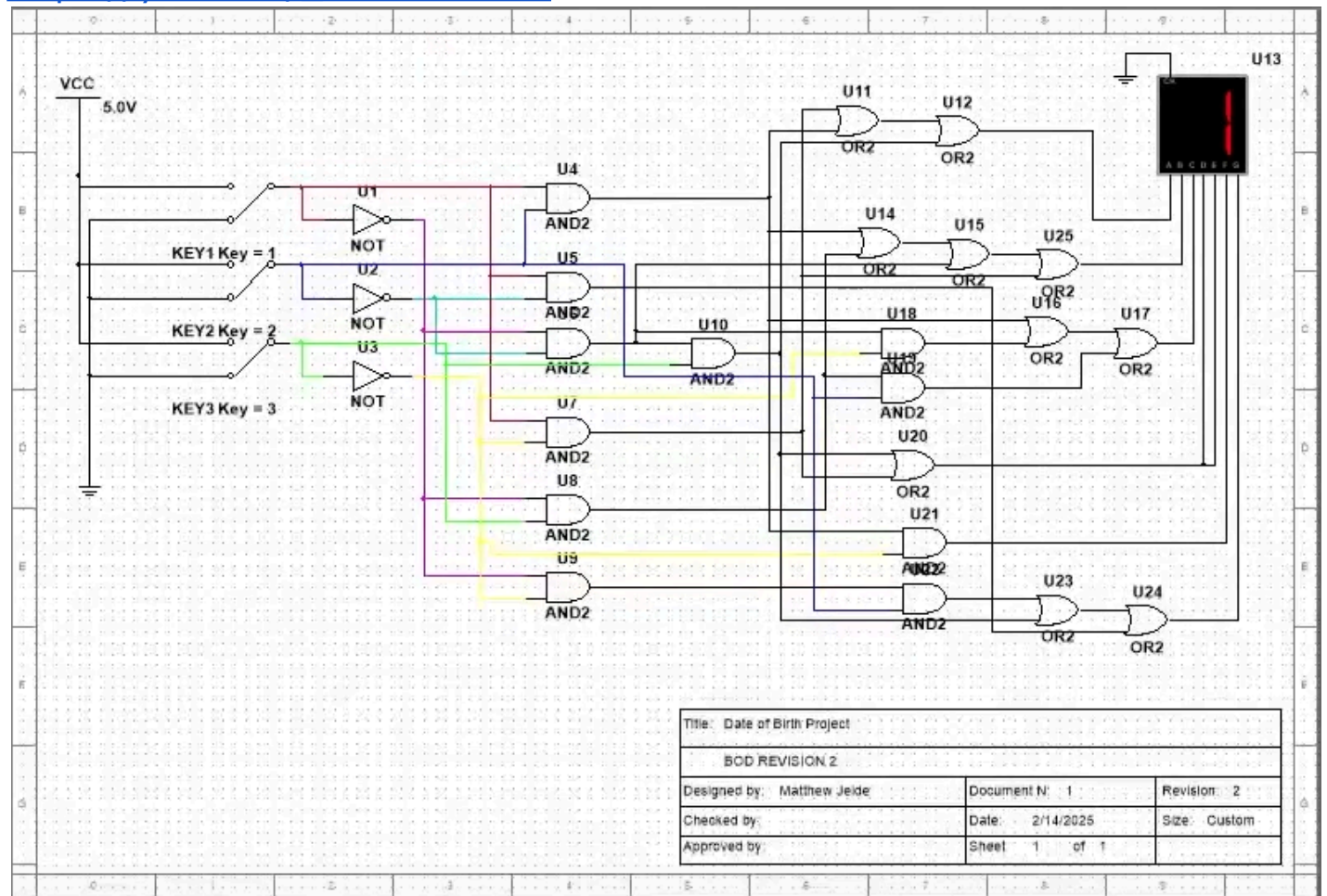

Prototyping

4. Using the DMS, build and test your Date of Birth design.

Jeide, Matthew

Date 2/7/2025

Period 2

- Verify that the circuit is working as designed. If it is not, do not change your design. You know that your design is good because you simulated it. If your circuit isn't working correctly, you must have built something incorrectly.
- Review your circuit implementation to identify your mistakes, make the necessary corrections, and retest.
- Be sure to document all changes in your engineering notebook.

Insert a video of your working breadboard design.

Not completed yet, document will be updated when that happens/

4. In the space provided below attach this completed worksheet to your E-Portfolio.

Insert your work on your E-Portfolio. Attach your E-Portfolio link here.
Make sure to include a video of the XOR and the XNOR adding the values.

<https://sites.google.com/riversideunified.org/matthewjeide/projects/de-2024-2025/date-of-birth-project>

Conclusion

Please answer in complete sentences. Minimum of three.

Write a conclusion (minimum 250 words) to describe the process that you used to design, simulate, and build your Date of Birth circuit. This conclusion must include all of your design work (truth table, K-Maps), preliminary and final schematics, parts list, and a digital photograph of your final circuit. The documentation should be complete enough that another student with the same knowledge of digital electronics could reproduce your design without any additional assistance.

Must write a 250-word conclusion explaining your design process, simulation, and how you built your Date of Birth Circuit.

The design and construction of the Date of Birth combinational logic circuit involved multiple key stages, including conceptualization, truth table development, Karnaugh map (K-Map) simplification, schematic design, simulation, and final prototyping.

The first step was to define the logic required to display a date of birth in MM-DD-YY format using a seven-segment display (SSD). This required determining the appropriate inputs and outputs. The three inputs (X, Y, Z) were designed to represent a binary count from 000 to 111, each corresponding to a segment display output. The truth table was developed to define the correct logic states for each of the seven segments (a through g) corresponding to the desired numerical outputs.

Once the truth table was established, Karnaugh maps were used to simplify the Boolean expressions for each segment. This step allowed us to minimize the number of required logic gates, improving efficiency and reducing hardware complexity. The resulting Boolean expressions dictated the selection and arrangement of logic gates in the circuit.

A preliminary schematic was developed using NI Multisim. The circuit incorporated various logic gate ICs, including the 74LS04 (Hex Inverter), 74LS08 (Quad AND), 74LS32 (Quad OR), 74LS00 (Quad NAND), and 74LS02 (Quad NOR) to implement the required logic functions.

Following schematic completion, the design was simulated within the CDS environment. This step ensured proper functionality before physical prototyping. Inputs were toggled to verify expected outputs, and minor logic refinements were made where necessary. Once simulation results confirmed correctness, the circuit was built on a breadboard using the specified ICs and wiring components.

During the prototyping stage, switches were used for the inputs X, Y, and Z to manually test the SSD display. The circuit will be meticulously wired according to the schematic, ensuring that each logic gate received the correct signals.

The final working circuit will be documented with a digital photograph, ensuring that future students could replicate the design. All design files, including the truth table, K-Maps, schematics, and component lists, were included in the project documentation. This comprehensive process ensured a fully functional Date of Birth combinational logic circuit and provided a clear methodology for others to follow.