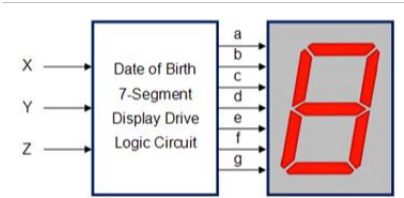


W6/7B: DE [SKETCH/MULTISIM BDAY] 2.4.1 Date of Birth Combinational Logic Circuit Design

Equipment

Calculator (preferably one with a number base conversion feature)  
Computer with Circuit Design Software (CDS)  
Breadboarding Hardware *or* Digital MiniSystem



- Integrated Circuits:
    - 74LS04 (Hex Inverter gates)
    - 74LS08 (Quad AND gates)
    - 74LS32 (Quad OR gates)
    - 74LS00 (Quad NAND gates)
    - 74LS02 (Quad NOR gates)
  - 22-gauge solid wire
  - Multipurpose Wire Stripper
1. Detailed Design Specifications:
- The SSD must be a common cathode.
  - Current limiting resistors (150 Ω — 270 Ω) must be used.
  - The Karnaugh mapping technique must be used to obtain the simplified logic expression for each of the seven segments.
  - At least one segment must be implemented with NAND only logic.
  - At least one segment must be implemented with NOR only logic.
  - The implementation of the remaining segments is your choice (XOR and XNOR) can be used and will save you time.

Insert Circuit Sketch- Work must have a stamp to get credit.

| Last Name | First Name | Middle Name | Suffix | Grd | Age | Birthdate  |
|-----------|------------|-------------|--------|-----|-----|------------|
| Jeide     | Matthew    | Alexander   | Jr     | 11  | 17  | 12/12/2007 |

Please be neat with your sketching. It makes it easier to make corrections if needed.

DOB Truth Table

| X | Y | Z | D |
|---|---|---|---|
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 2 |
| 0 | 1 | 0 | - |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 2 |
| 1 | 0 | 1 | - |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 7 |

| A | B | C | D | E | F | G |
|---|---|---|---|---|---|---|
| 0 | 1 | 1 | 0 | 0 | 0 | 0 |
| 1 | 1 | 0 | 1 | 1 | 0 | 1 |
| 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 1 | 1 | 0 | 0 | 0 | 0 |
| 1 | 1 | 0 | 1 | 1 | 0 | 1 |
| 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 | 0 | 0 |

RECEIVED  
FEB 11 2025

Segment A

| $\bar{X}$ | $\bar{Y}$ | Z |
|-----------|-----------|---|
| 0         | 0         | 1 |
| 0         | 0         | 0 |
| 1         | 1         | 1 |
| 1         | 1         | 0 |

$$X\bar{Z} + X\bar{Y} + \bar{X}\bar{Y}Z$$

Segment D B E

| $\bar{X}$ | $\bar{Y}$ | Z |
|-----------|-----------|---|
| 0         | 0         | 1 |
| 0         | 0         | 0 |
| 1         | 1         | 0 |
| 1         | 1         | 0 |

$$XZ + \bar{X}\bar{Y}Z$$

Segment B

| $\bar{X}$ | $\bar{Y}$ | Z |
|-----------|-----------|---|
| 1         | 1         | 1 |
| 0         | 0         | 1 |
| 1         | 1         | 1 |
| 1         | 1         | 0 |

$$\bar{X}\bar{Y} + \bar{X}Z + X\bar{Z} + XY$$

Segment F

| $\bar{X}$ | $\bar{Y}$ | Z |
|-----------|-----------|---|
| 1         | 1         | 0 |
| 1         | 1         | 1 |
| 1         | 1         | 0 |
| 1         | 1         | 1 |

$$XYZ$$

Segment C

| $\bar{X}$ | $\bar{Y}$ | Z |
|-----------|-----------|---|
| 1         | 0         | 1 |
| 0         | 0         | 1 |
| 1         | 1         | 1 |
| 0         | 0         | 0 |

$$XY + \bar{Z}\bar{X}\bar{Y} + Z\bar{X}\bar{Y}$$

Segment G


| $\bar{X}$ | $\bar{Y}$ | Z |
|-----------|-----------|---|
| 0         | 0         | 1 |
| 0         | 0         | 0 |
| 1         | 1         | 0 |
| 1         | 1         | 1 |

$$X\bar{Y} + \bar{X}\bar{Y}Z + \bar{X}\bar{Y}\bar{Z}$$

Jeide, Matthew

Date 2/14/2025

Period 2

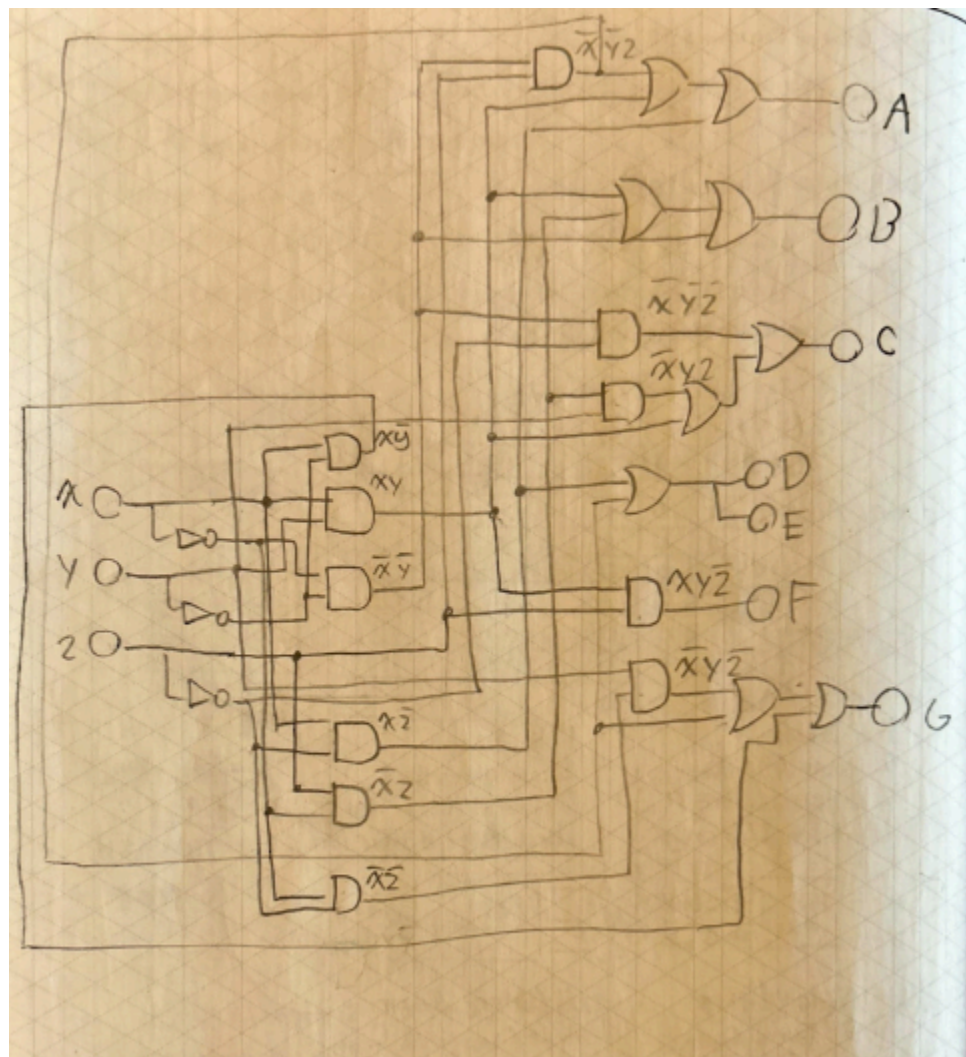

## Simulation

Using the Circuit Design Software (CDS), enter and test your Date of Birth design.

**WARNING: At least one segment must be implemented with AND, OR, NOR, and NAND. We don't have enough chips to use only one type of AOI Chip.**

- g. The implementation of the remaining segments is your choice.
- h. Use switches for the inputs X, Y, and Z.
- i. If two SSD pins share the same input, you may need to reduce the resistance to get the segment to display.
- j. Verify that the circuit is working as designed.
- k. If the circuit is not working properly, review your design work and circuit implementation to identify your mistake. Make any necessary corrections and retest.
- l. Be sure to document all changes in your engineering notebook.

Insert a screenshot and video of the Multisim design [EX: MM-DD-YY format]

Must include your name and date on the title block and the title of the assignment. Make sure to include a **PDF and a video.**

[https://www.youtube.com/watch?v=\\_6YM0bM2M5s](https://www.youtube.com/watch?v=_6YM0bM2M5s)



