

Truth Table Construction

- A truth table shows how the logic design output respond to all combinations of inputs
- A logic design with N inputs will have 2^N input combinations
- Truth table inputs are listed in ascending binary count order in the left-most columns
- Truth table output(s) are listed in columns to the right of the inputs where some logic circuits have more than one output

Constructing A Truth Table

INPUTS			Output
X	Y	Z	F ₁
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

Input Combinations
3-Inputs
8-combinations
 $8=2^3$

Outputs for each
input combination

Truth table to Logic Expression

- Write a minterm adjacent to every row in the truth table that contains a one in the output column
- Write the Sum-of-products (SOP) logic expression by summing all of the minterms

$$F_5 = \bar{X}\bar{Y}Z + \bar{X}YZ + X\bar{Y}\bar{Z} + XY\bar{Z}$$

SOP Logic Expression

Truth Table to Logic Expression Example

$$F_6 = \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}CD + \bar{A}B\bar{C}D + A\bar{B}\bar{C}D + ABCD$$

$$F_7 = \bar{X}\bar{Y}\bar{Z} + XZ + \bar{X}\bar{Y}Z$$

Design Specifications to Truth Table

1. Identify the number of variables
2. Assign variable names and establish the assignment condition for each variable
e.g. what does a 0 or 1 mean for that input?
3. Create a truth table

Signature: *Elvira Jick*

Date: *1/16/21*

Team Members: _____

Witness: _____

Date: _____

Example

P: Pressure Sensor $\rightarrow 0 = \text{Safe} / 1 = \text{Unsafe}$ T: Temperature Sensor $\rightarrow 0 = \text{Safe} / 1 = \text{Unsafe}$ A: Alarm $\rightarrow 0 = \text{Alarm off} / 1 = \text{Alarm on}$

P	T	A
0	0	0
0	1	1
1	0	1
1	1	1

Example #2

W: Window sensor $\rightarrow 0 = \text{Off} / 1 = \text{On Open}$ D: Door sensor $\rightarrow 0 = \text{Closed} / 1 = \text{Open}$ K: Key $\rightarrow 0 = \text{No key} / 1 = \text{Key}$

$$S = \overline{K} \overline{D} + \overline{K} W$$

11/11/24

Signature

[Signature]

Date

11/11/24

Team Members:

Witness:

Date:

Continued From Page #

35

Continued On Page #