

CONCLUSION

①

C, since Base 8 is smaller than Base 10, an equivalent in Base 8 would have to be greater than its counterpart in Base 10, meaning B.A is additionally not a valid octal number.

1/98/25

Current Given

②

The chapter does not understand Hexadecimal.

Seven Segment Display Notes

Segment Identification


A Seven-Segment Display (SSD) is simply a figure 8 grouping of LEDs and some include a decimal point (DP).

Each segment is labeled (a) through (g)

SSDs can function in two configurations

Common Cathode (all LED cathodes are connected)

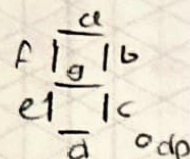
Common Anode (all LED anodes are connected)




SSDs have limited display capabilities, only a select few alpha characters can possibly be displayed

Basic LED Operations

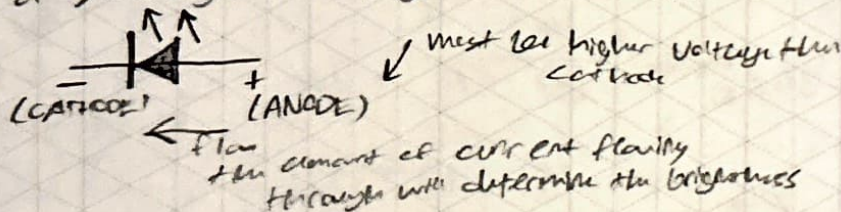Understanding how a seven segment display works requires knowing how an LED is powered



LED Anode at 5 Volts

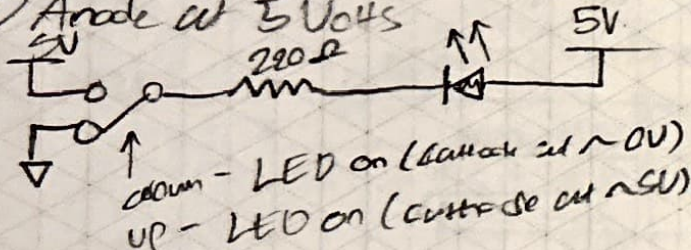

Larger resistors will limit more current, meaning a dimmer LED.

Smaller resistors will limit less current, meaning a brighter LED.

Signature: *Current Given*

Date: 1/98/25


Team Members:

Witness:

Date:

An anode SSD will activate segments IF connected to ground

LED Cathode at 0V

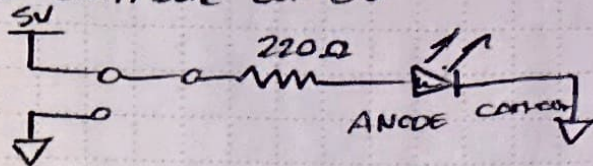

On - Anode at 5V,
Cathode at 0V
Off - Anode at 0V,
Cathode at 0V

A cathode SSD will activate segments IF connected to VCC

Resistor Values for SSD

The resistor value determines the amount of current that flows through the SSD LEDs

The amount of current determines the brightness of an LED

- Too little current, you can't see the LED
- Too much current, the LED might be damaged

To know the correct value, read the data sheet for the SSD.

Circuit Theory Review

The voltage across the LED when on is 1.5V

Use Kirchhoff's Voltage Law to calculate a 3.5V across the resistor

$$5V - 1.5V = 3.5V$$

Use Ohm's Law to calculate the value of the resistor using the current through the LED

$$R = \frac{3.5V}{I}$$

$$= \frac{3.5V}{15mA} = 233.33\Omega = 220\Omega \text{ (standard value)}$$

Signature: [Signature]

Date: 1/28/24

Team Members:

Witness:

Date:

Continued From Page # 32

Continued On Page #