

Design Specifications

Design a combinational logic circuit with the following specifications:

Three (3) inputs and (7) seven outputs.

As inputs count 000 to 111, the outputs (a-g) displays a date of birth (DOB) on a 7-segment display

The 7-segment display is a common anode display

The DOB will be displayed in a MM-DD-YY format

DOB Truth Table

X	Y	Z	D
0	0	0	1
0	0	1	2
0	1	0	-
0	1	1	1
1	0	0	2
1	0	1	-
1	1	0	0
1	1	1	7

A	B	C	D	E	F	G
0	1	1	0	0	0	0
1	1	0	1	1	0	1
0	0	0	0	0	0	1
0	1	1	0	0	0	0
1	1	0	1	1	0	1
0	0	0	0	0	0	1
1	1	1	1	1	1	0
1	1	1	0	0	0	0

Segment A

\bar{X}	\bar{Y}	Z
0	0	1
0	0	0
1	1	1
1	1	0

$$X\bar{Z} + XY + \bar{X}\bar{Y}Z$$

Segment B

\bar{X}	\bar{Y}	Z
1	1	1
1	0	1
1	1	1
1	0	1

$$Z + XY + \bar{X}\bar{Y}$$

Segment C

\bar{X}	\bar{Y}	Z
1	0	0
1	0	1
1	1	1
1	0	0

$$XY + \bar{Z}\bar{X}\bar{Y} + Z\bar{X}\bar{Y}$$

Segment D B E

\bar{X}	\bar{Y}	Z
0	1	1
0	1	0
1	1	0
1	1	0

$$X\bar{Z} + \bar{X}\bar{Y}Z$$

Segment F

$$XY\bar{Z}$$

Segment G

\bar{X}	\bar{Y}	Z
0	1	1
0	1	0
1	0	0
1	1	1

$$X\bar{Y} + \bar{X}Y\bar{Z} + \bar{X}\bar{Y}Z$$

Signature: Enam JinnDate: 2/10/25

Team Members:

Witness:

Date:

Continued From Page #

Continued On Page #