

Karnaugh Mapping (K-mapping)

K-maps are a graphical technique used to simplify a logic equation.

K-maps are procedural and much clearer than boolean simplification.

K-maps can be used for any number of input variables, but are only practical for two, three, and four variables.

K-map format

Each minterm in a truth table corresponds to a cell in the K-map.

K-map cells are labeled where horizontal and vertical movement steps change by one variable.

This allows simpler term grouping in a sum-of-products expression.

The SOP expression of the logic function can be obtained by OR-ing together cells or cell groups that contain 1s.

Adjacent Cell Simplification Two Variable K-Map

	\bar{X}	X
\bar{W}	1	0
W	1	0

\bar{X}

	\bar{X}	X
\bar{W}	1	0
W	1	0

Groups of one — 4 possibilities
 Groups of two — 4 possibilities
 Groups of four — 1 possibility

Procedure

1. Construct a table for the K-map
2. Place 1's in cells that correspond to 1's in the truth tables
3. Place 0's in other cells
4. Identify and group all isolated 1's
5. Group any hexet
6. Group any octet, or even if it contains 1's already grouped but not enclosed
7. Group any quad, \downarrow
8. Group any pair
9. Or together all terms to generate the SOP equation.

Signature: *Amrutha Jide*

Date: 12/3

Team Members:

Witness:

Date:

Continued From Page #

Continued On Page #

①

$$\begin{array}{c|c} \bar{K} & \bar{J} \\ \hline K & J \end{array}$$

$$\begin{array}{cc} 1 & 0 \\ 1 & 0 \end{array}$$

$$\bar{J}$$

②

$$\begin{array}{cc} \bar{W} & X \\ \hline W & X \end{array}$$

$$\begin{array}{cc} 1 & 0 \\ 0 & 0 \\ 0 & 1 \\ 1 & 0 \end{array}$$

③

$$\begin{array}{cc} \bar{E} & F \\ \hline E & F \end{array}$$

$$\begin{array}{cc} 0 & 1 \\ 1 & 0 \\ 0 & 1 \\ 1 & 0 \end{array}$$

FG

$\bar{F}\bar{G}$

$F\bar{G} + \bar{F}G$

Matthew Jelske 12/13

Signature:

Date:

Team Members:

Witness:

Date:

Continued From Page #

Continued On Page #